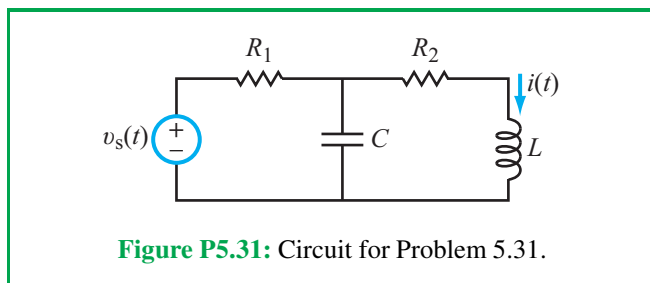


**Problem 5.31** The circuit in Fig. P5.31 is excited by the source waveform shown in Fig. P5.26(b).



- Derive Fourier series representation of  $i(t)$ .
- Calculate the first five terms of  $v_{\text{out}}(t)$  using  $R_1 = R_2 = 100 \Omega$ ,  $L = 1 \text{ mH}$ , and  $C = 1 \mu\text{F}$ .
- Plot  $i(t)$  and  $v_s(t)$  using  $n_{\text{max}} = 100$ .

**Solution:** From Problem 5.25, the phasor domain presentation of  $v_s(t)$  is

$$\mathbf{V}_s = 6 + \sum_{n=1}^{\infty} \frac{8[1 - \cos(n\pi)]}{n\pi} e^{j90^\circ}.$$

Next, transfer function of circuit:

$$\text{define } \mathbf{Z}_1 = \frac{1}{j\omega C}, \quad \mathbf{Z}_2 = j\omega L.$$

Then following the derivation in Problem 5.25,

$$\begin{aligned} \mathbf{H} &= \frac{\mathbf{I}}{\mathbf{V}_s} = \frac{\mathbf{Z}_1}{(R_1 + \mathbf{Z}_1)(\mathbf{Z}_1 + \mathbf{Z}_2 + R_2) - \mathbf{Z}_1^2} \\ &= \frac{\frac{1}{j\omega C}}{\left(R_1 + \frac{1}{j\omega C}\right)\left(\frac{1}{j\omega C} + j\omega L + R_2\right) - \left(\frac{1}{j\omega C}\right)^2} \\ &= \frac{1}{(1 + j\omega CR_1)\frac{(1 - \omega^2 LC + j\omega CR_2)}{j\omega C} - \frac{1}{j\omega C}} \\ &= \frac{j\omega C}{(1 - \omega^2 LC) + j\omega C[R_2 + (1 - \omega^2 LC)R_1] - \omega^2 C^2 R_1 R_2 - 1} \\ \mathbf{H}(\omega) &= \frac{j}{j[R_2 + R_1(1 - \omega^2 LC)] - \omega(L + CR_1 R_2)} \\ &= \frac{1}{\sqrt{\omega^2(L + CR_1 R_2)^2 + [R_2 + R_1(1 - \omega^2 LC)]^2}} \\ &\quad \cdot \exp\left\{j90^\circ - \tan^{-1}\left[-\frac{R_2 + R_1(1 - \omega^2 LC)}{\omega(L + CR_1 R_2)}\right]\right\} \end{aligned}$$

and

$$\mathbf{H}(\omega = 0) = \frac{1}{R_1 + R_2}.$$

The phasor domain presentation of the current  $\mathbf{I}$ :

$$\mathbf{I}(\omega) = \frac{6}{R_1 + R_2} + \sum_{n=1}^{\infty} \frac{8[1 - \cos(n\pi)]}{n\pi} \frac{1}{\sqrt{n^2 \omega_0^2 (L + CR_1R_2)^2 + [R_2 + R_1(1 - n^2 \omega_0^2 LC)]^2}} \\ \times \exp \left\{ j180^\circ - \tan^{-1} \left[ -\frac{R_2 + R_1(1 - \omega^2 LC)}{\omega(L + CR_1R_2)} \right] \right\},$$

and in time domain:

$$i(t) = \frac{6}{R_1 + R_2} + \sum_{n=1}^{\infty} \frac{8(1 - \cos n\pi)}{n\pi} \frac{1}{\sqrt{n^2 \omega_0^2 (L + CR_1R_2)^2 + [R_2 + R_1(1 - n^2 \omega_0^2 LC)]^2}} \\ \times \cos \left( n\omega_0 t + 180^\circ - \tan^{-1} \left\{ -\frac{[R_2 + R_1(1 - \omega^2 LC)]}{\omega(L + CR_1R_2)} \right\} \right).$$

(b) Substituting the values of circuit components, the first five terms of  $i(t)$  are

$$\begin{aligned} n = 1 & \rightarrow 0.0252 \cos(\omega_0 t + 80^\circ) \\ n = 2 & \rightarrow 0 \\ n = 3 & \rightarrow 0.0078 \cos(3\omega_0 t + 61.5^\circ) \\ n = 4 & \rightarrow 0 \\ n = 5 & \rightarrow 0.0041 \cos(5\omega_0 t + 45.4^\circ) \end{aligned}$$

(c)

