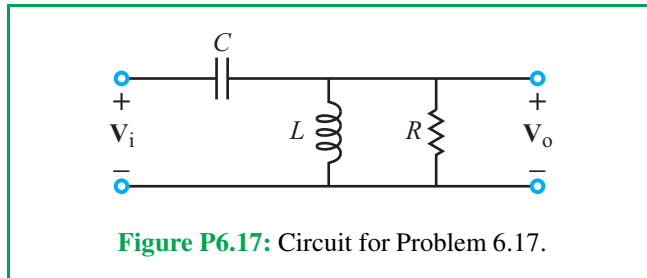


**Problem 6.17** For the circuit shown in Fig. P6.17 provide the following:

- An expression for  $\mathbf{H}(\omega) = \mathbf{V}_o/\mathbf{V}_i$  in standard form.
- Spectral plots for the magnitude and phase of  $\mathbf{H}(\omega)$ , given that  $R = 10 \Omega$ ,  $L = 1 \text{ mH}$ , and  $C = 10 \mu\text{F}$ .
- The cutoff frequency  $\omega_c$  and the slope of the magnitude (in dB) when  $\omega/\omega_c \ll 1$ .



**Solution:**

(a) Voltage division yields

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{(R \parallel j\omega L)}{1/j\omega C + (R \parallel j\omega L)} \\ &= \frac{-\omega^2 LC}{1 + j\omega L/R + j^2\omega^2 LC} \\ &= \frac{-(\omega/\omega_c)^2}{1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2}, \end{aligned}$$


with

$$\omega_c = \frac{1}{\sqrt{LC}}, \quad \xi = \frac{\omega_c L}{2R}.$$

(b) For  $R = 10 \Omega$ ,  $L = 1 \text{ mH}$ , and  $C = 10 \mu\text{F}$ ,

$$\omega_c = 10^4 \text{ rad/s}, \quad \xi = 0.5.$$

Spectral plots of  $M$  [dB] and  $\phi(\omega)$  are shown in Figs. P6.17(a) and (b).

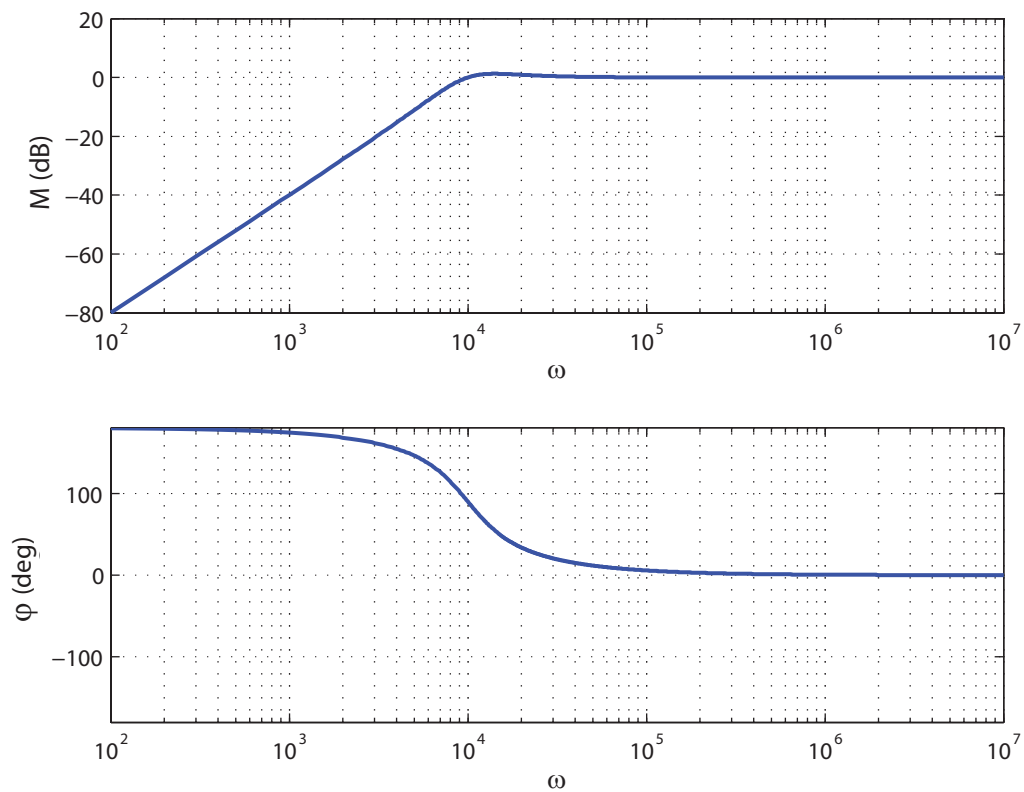**Figures P6.17(a) and (b)**

(c) For  $\omega/\omega_c \ll 1$ ,

$$\mathbf{H}(\omega) \approx -\left(\frac{\omega}{\omega_c}\right)^2 \quad \Rightarrow \quad \text{slope} = +40 \text{ dB/decade.}$$