

**Concept Question 4-10:** How does feedback provide immunity to op-amp dc gain variations with temperature?

The closed-loop dc gain is about  $1/K$  and the closed-loop bandwidth is about  $10^7 K$ , where  $K$  is the feedback factor, independent of the open-loop dc gain.