

Concept Question 4-5: Why is it preferable to use integrators rather than differentiators when using op-amp circuits to model desired transfer functions?

Because differentiators amplify noise, while integrators reduce noise. See Example 3-12.