

Concept Question 6-2: Are active filters used mostly at frequencies below 1 MHz or above 1 MHz?

Below 1 MHz, since op-amps do not always perform reliably at frequencies above 1 MHz. This is one advantage of passive filters.