

**Concept Question 6-3:** Why is it more practical to cascade multiple stages of active filters than to cascade multiple stages of passive filters?

Cascading multiple stages of passive filters can cause problems with the output impedance of one stage affecting the input of the following stage (loading) or impedance matching. Cascading active filters avoid these issues by using buffers between stages.